

EMBS Hardware Circuits – Equation Sheet



Symbols & Units

- **V** = Voltage (Volts, **V**, mV, μ V)
- **I** = Current (Amperes, **A**, mA, μ A)
- **R** = Resistance (Ohms, **Ω** , k Ω , M Ω)
- **Q** = Charge (Coulombs, **C**)
- **C** = Capacitance (Farads, **F**, μ F, nF, pF)
- **f** = Frequency (Hertz, **Hz**)
- **f_c** = Cutoff frequency (Hz)
- **R_{in}**, **R_f** = Input and feedback resistors (Ω)



Ohm's Law

$$V = I \cdot R$$

- Voltage = Current $\times$ Resistance.
- Used to size resistors, check circuit behavior.

Kirchhoff's Laws

KCL (Current Law):

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

At a node, total current in = total current out.

KVL (Voltage Law):

$$\sum V_{\text{loop}} = 0$$

- Around a loop, voltage rises = voltage drops.
-

Voltage Divider

$$V_{\text{out}} = V_{\text{in}} \cdot (R_2 / R_1 + R_2)$$

- Scales down a voltage (e.g., sensor output into ADC).
-

Capacitors

Charge:

$$Q = C \cdot V$$

Current–Voltage Relationship:

$$I(t) = C \cdot (dV(t) / dt)$$

- Capacitors block DC, pass AC (used for filtering biosignals).
 - Current through capacitor = capacitance * change in voltage over time
-

RC Low-Pass Filter

(Cuts out high-frequency noise, passes slow/biological signals)

$$f_c = 1 / 2\pi RC$$

- f_c = cutoff frequency
 - R = resistance in Ohms
 - C = capacitance in Farads
-

RC High-Pass Filter

(Removes baseline drift, passes faster changes)

$$f_c = 1 / 2\pi RC$$

- f_c = cutoff frequency
 - R = resistance in Ohms
 - C = capacitance in Farads
-

Operational Amplifier (Op-Amp)

Gain:

$$\text{Gain} = V_{\text{out}} / V_{\text{in}}$$

- V_{out} = output voltage amplitude
- V_{in} = input voltage amplitude

Inverting Amplifier:

$$V_{\text{out}} = -(R_f / R_{\text{in}}) V_{\text{in}}$$

Non-Inverting Amplifier:

$$V_{\text{out}} = (1 + R_f / R_{\text{in}}) V_{\text{in}}$$

Buffer (Voltage Follower):

$$V_{\text{out}} = V_{\text{in}}$$
